

### Homework 3

1) a)  $P(C_1) = P(a) \cdot P(b) = 0.5 \times 0.25 = 0.125$

~~$P(C_2) = P(c) - (P(c) \cdot P(d)) = 1 - (0.75 \times 0.5) =$~~

$P(C_2) = 1 - (\overline{P(c)} \cdot \overline{P(d)}) = 1 - ((1 - 0.75)(1 - 0.5)) = 0.875$

$P(C_3) = P(C_1) \cdot P(C_2) = 0.125 \times 0.875 = 0.109375$

$P(C_4) = 1 - P(C_3) = 1 - 0.109375 = 0.890625$

b)  $\alpha(C_1) = P(C_1) \cdot \overline{P(C_1)} = 0.109375$

$\alpha(C_2) = P(C_2) \cdot \overline{P(C_2)} = 0.109375$

$\alpha(C_3) = P(C_3) \cdot \overline{P(C_3)} = 0.0974$

$\alpha(C_4) = P(C_4) \cdot \overline{P(C_4)} = 0.0974$

c)  $P_{\text{switching}}(C_1) = \alpha(C_1) \cdot C_1 \cdot V_{DD}^2 \cdot f$   
 $= 0.109375 \times 2 \times 10^{-6} \times 1.2^2 \times 2.5 \times 10^9 = 787.5 \text{ W}$

$P_{\text{switching}}(C_2) = 0.109375 \times 5 \times 10^{-6} \times 1.2^2 \times 2.5 \times 10^9 = 1968.75 \text{ W}$

~~$P_{\text{switching}}(C_3) = 0.0974 \times 0.5 \times 10^{-6} \times 1.2^2 \times 2.5 \times 10^9 = 175.32 \text{ W}$~~

$P_{\text{switching}}(C_4) = 0.0974 \times 17 \times 10^{-6} \times 1.2^2 \times 2.5 \times 10^9 = 5960.88 \text{ W}$

d)  $P_{\text{total}} = 787.5 \text{ W} + 1968.75 \text{ W} + 175.32 \text{ W} + 5960.88 \text{ W} = 8892.45 \text{ W}$

a) You can either use power gating ~~or clock gating~~ to disconnect the voltage ~~or~~ clock source from the circuit when it is dormant, or operate at a lower voltage (e.g. 50% of  $V_{DD}$ ) or reduce the transistor width.

b) By operating at a lower  $V_{DD}$ , e.g. 50% of  $V_{DD} \rightarrow \text{Power} \propto \frac{\text{Voltage}^2}{R}$


$$\frac{\text{Power}_{\text{new}}}{\text{Power}_{\text{old}}} = \frac{\text{Voltage}_{\text{new}}^2}{\text{Voltage}_{\text{old}}^2} = \frac{(0.5 V_{DD})^2}{V_{DD}^2} = 0.5^2 = 0.25$$

Power savings =  $1 - 0.25 = 0.75$  (75%)

Assuming the circuit is idle 50% of the time, Savings =  $(75\%)(50\%) = 37.5\%$

c) Power gating circuit is needed leading to added area and delay. Also, for the operation at 50% of  $V_{dd}$  requires Voltage domain crossing circuitry. Finally, by reducing the transistor width, you have less drive for the transistor leading to longer latency.

3.) 1 stage




$$D = 1 \times 100 + 1 = 101$$

$$E \propto C_{tot} = (2 \times 1) + 100 = 102$$

$$EDP \propto 101 \times 102 = 10302$$

2 stages

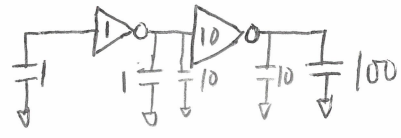


$$D = 2 \times \sqrt{100} + 2 = 22$$

$$E \propto C_{tot} = (2 \times 1) + (2 \times 10) + 100 = 122$$

$$EDP \propto 22 \times 122 = 2684$$

3 stages

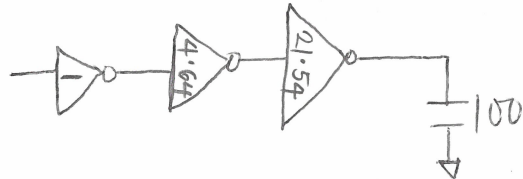


$$D = 3 \times \sqrt[3]{100} + 3 = 16.92$$

$$E \propto C_{tot} = 2(1 + 4.64 + 21.54) + 100 = 154.36$$

$$EDP \propto 16.92 \times 154.36 = \boxed{2611.77}$$

4 stages

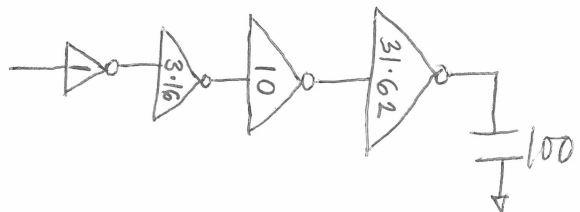

$$D = 4 \times \sqrt[4]{100} + 4 = 16.65$$

$$E \propto C_{tot} = 2(1 + 3.16 + 10 + 31.62) + 100 = 191.56$$



$$EDP \propto 16.62 \times 191.56 = 3183.73$$

Minimum EDP occurs for 3 stages.

4)


	L doubles	W doubles	d doubles	h doubles	E doubles	P doubles
R	doubles	halves	-	halves	-	doubles
L	doubles	non-linear	-	non-linear	-	-
C	doubles	-	halves	doubles	doubles	-

5) 1 stage.

  


$$D = (1C \times 1R) + (100C \times 3R) = RC + 300RC = 301RC = 301\tau$$

2 stages

 

$$D = (1C \times 1R) + (10C \times 3R) + (10C \times \frac{R}{10}) + (100C \times \frac{21}{10}R) = RC + 30RC + RC + 210RC = 242RC = 242\tau$$

3 stages

 

$$\text{Delay} = RC \left[ (1 \times 1) + (3 \times 4.64) + (4.64 \times \frac{1}{4.64}) + (21.54 \times 2.216) + (21.54 \times \frac{1}{21.54}) + (100 \times 2.046) \right]$$

$$= 269.25RC = 269.25\tau$$

Minimum<sub>delay</sub> = 2 stages.