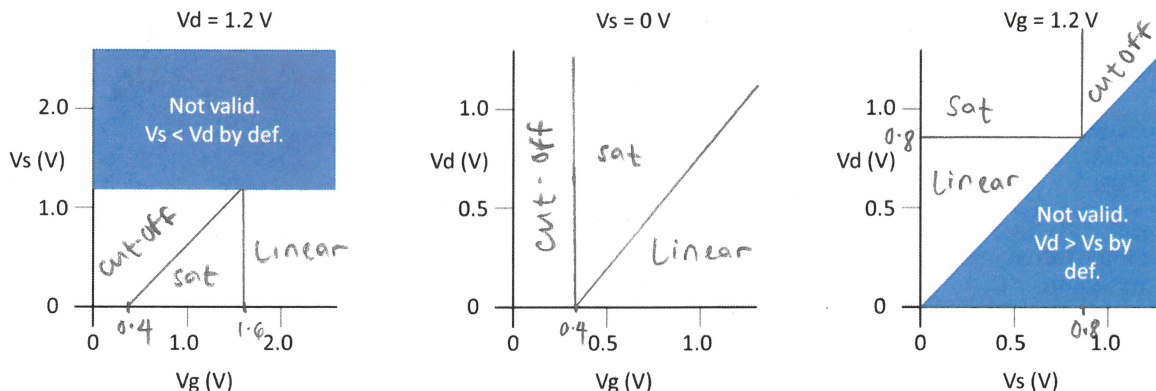



- 20 1. In an NMOS transistor, $V_{tn} = 0.4$ V. Sketch the regions of operation when one of the voltages is held constant. What do you notice?



- 10 2. N-type Si has better carrier transport properties than P-type Si, so why don't we use NMOS for all of our logic?





P-type silicon is needed in using PMOS for the pull-up because NMOS is bad in transmitting 1.

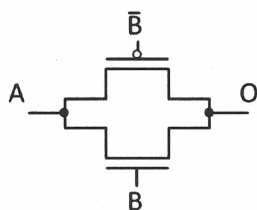- 10 3. In the following diagram, describe the function of the shown gate (A and B are the inputs)? Why do we need both NMOS and PMOS?




This is a transmission gate or T-gate or Pass gate. The NMOS will be used to pass 0 from 'A' to 'O' when $A = 0$ and the PMOS will be used to pass 1 from 'A' to 'O' when $A = 1$.

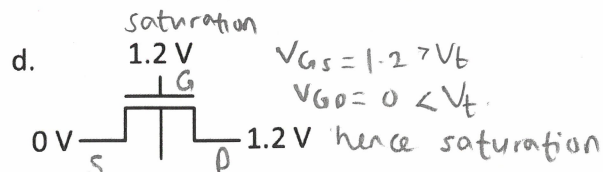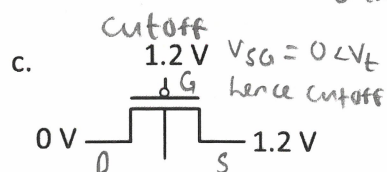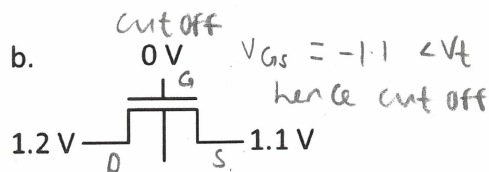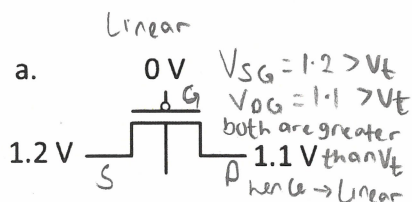- 10 4. In which operating regions are the following transistors ($v_{tn} = -v_{tp} = 0.4$ V), and identify the terminals (assume there is no leakage and no body effect)?






20 5. Calculate V_o in the following circuit when: (assume $V_{tp} = 0.4 \text{ V}$ and R is large)

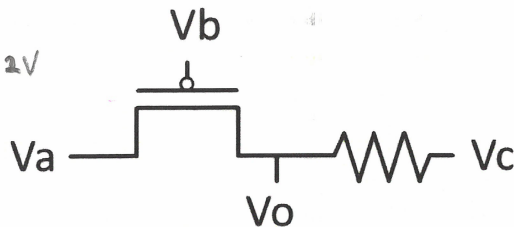- a. $V_a = 0 \text{ V}$, $V_b = 1.2 \text{ V}$, $V_c = 1.2 \text{ V}$
cutoff, hence $V_o = V_c = 1.2 \text{ V}$
b. $V_a = 1.2 \text{ V}$, $V_b = 0 \text{ V}$, $V_c = 0 \text{ V}$
on, since pmos passes 1 fully, $V_o = V_a = 1.2 \text{ V}$
c. $V_a = 0 \text{ V}$, $V_b = 0 \text{ V}$, $V_c = 1.2 \text{ V}$
 $V_o = 0.4 \text{ V}$, When pmos passes 0,
it drags V_{DD} to $V_{tp} = 0.4 \text{ V}$



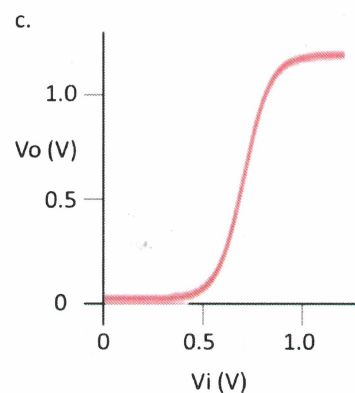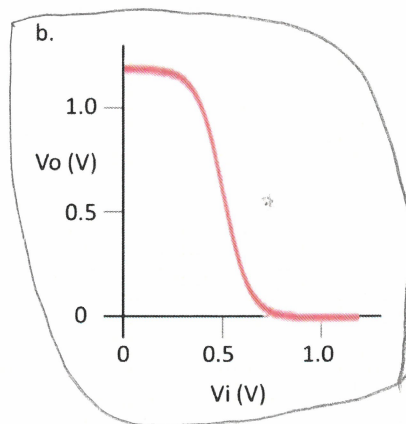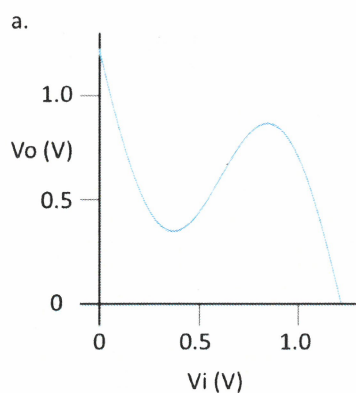10 6. Pick the transfer characteristics which describe a stable inverter. Why is it so important that an inverter chain be stable? Because it reduces noise



20 7. In the selected stable graph from Q6 if at V_i an input of '1' is represented by a voltage in $[0.8 \text{ V}, 1.2 \text{ V}]$ and an input '0' is represented by a voltage in $[0 \text{ V}, 0.5 \text{ V}]$, then in the inverter chain below, what are the possible output ranges at V_1 ? What are the possible output ranges at V_2 ? What are the possible output ranges at V_3 .

