

1: In the circuit shown, assume all switching activity is uncorrelated.  $P_a$  (the probability that at any clock cycle input  $a$  is a logic '1') = 0.5.  $P_b = 0.25$ .  $P_c = 0.75$ .  $P_d = 0.5$ .

- Calculate the probabilities of all nodes in the circuit.
- Calculate the activity factor ( $\alpha$ ) of every node in the circuit.
- Assuming the clock frequency is 2.5 GHz,  $V_{dd} = 1.2$  V,  $C_1 = 2 \mu F$ ,  $C_2 = 5 \mu F$ ,  $C_3 = 0.5 \mu F$ ,  $C_4 = 17 \mu F$ , calculate the average switching power used to drive each capacitor.
- Calculate the overall switching power consumed by the circuit.


 


TABLE 5.1 Switching probabilities

Gate	$P_Y$
AND2	$P_A P_B$
AND3	$P_A P_B P_C$
OR2	$1 - \bar{P}_A \bar{P}_B$
NAND2	$1 - P_A P_B$
NOR2	$\bar{P}_A \bar{P}_B$
XOR2	$P_A \bar{P}_B + \bar{P}_A P_B$

$$P_a = 0.5 \quad P_c = 0.75$$

$$P_b = 0.25 \quad P_d = 0.5$$

 

$$P_{n1} = P_a \text{ and } P_b$$

$$= 0.5(0.25) = \boxed{0.125}$$

$$P_{n2} = P_c \text{ or } P_d = 1 - \bar{P}_c \bar{P}_d$$

$$= 1 - (1 - 0.75)(1 - 0.5) = 1 - (0.25)(0.5) = \boxed{0.875}$$

$$P_{n3} = P_{n1} \text{ and } P_{n2}$$

$$= 0.125(0.875) = \boxed{0.109375}$$

$$P_{n4} = 1 - P_{n3}$$

$$= 1 - 0.109375 = \boxed{0.890625}$$

b)  $\alpha = \bar{p} \cdot p$

$$\alpha_{P_{n1}} = (0.125)(1-0.125) = \boxed{0.109375}$$

$$\alpha_{P_{n2}} = (0.875)(1-0.875) = \boxed{0.109375}$$

$$\alpha_{P_{n3}} = (0.109375)(1-0.109375) = \boxed{0.097412109}$$

$$\alpha_{P_{n4}} = (0.890625)(1-0.890625) = \boxed{0.097412109}$$

c)  $P = \alpha \cdot f \cdot C \cdot V^2$

$$C_1 = 2 \mu F, C_2 = 5 \mu F, C_3 = 0.5 \mu F, C_4 = 17 \mu F,$$

$$V_{dd} = 1.2V, \text{ clock freq.} = 2.5 \text{ GHz} = 2.5 \cdot 10^9 \text{ Hz}$$

$$P_{C1} = (0.109375)(2.5 \times 10^9)(2 \cdot 10^{-6})(1.2)^2$$

$$= \boxed{787.5 \text{ W}}$$

$$P_{C2} = (0.109375)(2.5 \times 10^9)(5 \cdot 10^{-6})(1.2)^2$$

$$= \boxed{1968.75 \text{ W}}$$

$$P_{C3} = (0.097412109)(2.5 \times 10^9)(0.5 \cdot 10^{-6})(1.2)^2$$

$$= \boxed{175.34 \text{ W}}$$

$$P_{C4} = (0.097412109)(2.5 \times 10^9)(17 \cdot 10^{-6})(1.2)^2$$

$$= \boxed{5961.62 \text{ W}}$$

d)

$$\begin{aligned} P_{\text{total}} &= P_{C1} + P_{C2} + P_{C3} + P_{C4} \\ &= 787.5 + 1968.75 + 175.34 + 5961.62 \\ &= \boxed{8893.2 \text{ W}} \end{aligned}$$

**2: In a given computer, block X consumes 50% of the total static power, but it is only operational in bursts 10% of the time.**

- a) Describe two methods for reducing the static power used by block X.
- b) Estimate the power savings for your chosen methods.
- c) Describe any drawbacks for your methods.

a) You can either use power gating ~~or clock gating~~ to disconnect the voltage ~~or~~ clock source from the circuit when it is dormant. or operate at a lower voltage (e.g 50% of  $V_{dd}$ ) or reduce the transistor width.

b) By operating at a lower  $V_{dd}$ , e.g 50% of  $V_{dd} \rightarrow \text{Power} \propto \frac{\text{Voltage}^2}{R}$

$$\frac{\text{Power}_{\text{new}}}{\text{Power}_{\text{old}}} = \frac{\text{Voltage}_{\text{new}}^2}{\text{Voltage}_{\text{old}}^2} = \frac{(0.5 V_{dd})^2}{V_{dd}^2} = 0.5^2 = 0.25$$


$$\text{Power savings} = 1 - 0.25 = 0.75 (75\%)$$

Assuming the circuit is idle 50% of the time, savings =  $(75\%)(50\%) = 37.5\%$

c) Power gating circuit is needed leading to added area and delay. Also, for the operation at 50% of  $V_{dd}$  requires voltage domain crossing circuitry. Finally, by reducing the transistor width, you have less drive for the transistor leading to longer latency.

3: In HW2 Q4, we asked you to find the optimal number of inverters minimize delay to drive a 100-unit load starting with a unit inverter. Repeat the problem now minimizing the switching energy delay product (EDP) under a constant  $V_{dd}$ ,  $f$ , and  $\alpha$ . The diffusion nodes are disconnected because the inverters in the cascade are sized differently.

3.) 1 stage




$$D = 1 \times 100 + 1 = 101$$

$$E \propto C_{tot} = (2 \times 1) + 100 = 102$$

$$EDP \propto 101 \times 102 = 10302$$

2 stages

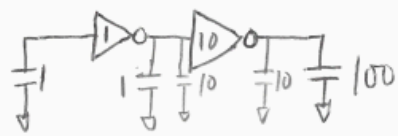


$$D = 2 \times 2\sqrt{100} + 2 = 22$$

$$E \propto C_{tot} = (2 \times 1) + (2 \times 10) + 100 = 122$$

$$EDP \propto 22 \times 122 = 2684$$

3 stages

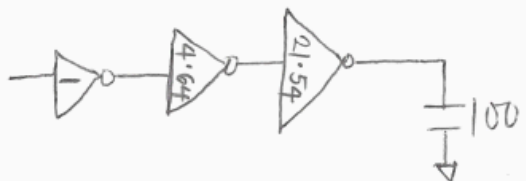


$$D = 3 \times 3\sqrt{100} + 3 = 16.92$$

$$E \propto C_{tot} = 2(1 + 4.64 + 21.54) + 100 = 154.36$$

$$EDP \propto 16.92 \times 154.36 = \boxed{2611.77}$$

4 stages

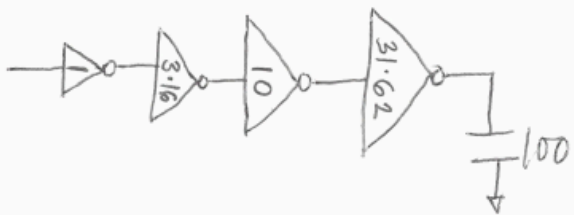


$$D = 4 \times 4\sqrt{100} + 4 = 16.65$$

$$E \propto C_{tot} = 2(1 + 3.16 + 10 + 31.62) + 100 = 191.56$$

$$EDP \propto 16.62 \times 191.56 = 3183.73$$

Minimum EDP occurs for 3 stages.

 **4:** In the shown interconnect model, two wires are placed adjacent to each other with length  $l$ , thickness  $h$ , width  $w$ , and are space a distance of  $d$  apart. A dielectric of permittivity  $\epsilon$  encases the wires which have a resistivity of  $\rho$ . Current flows along the length of the conductor as shown. **Fill in the table analyzing the effect of material parameters and dimensions on resistance (R), capacitance (C), and inductance (L)** (assuming all parameters are constant except for the one listed).



	l doubles	w doubles	d doubles	h doubles	$\epsilon$ doubles	$\rho$ doubles
R:						
L:						
C:						

$$R = \rho \cdot \frac{l}{w \cdot h}$$

$\rho, l$  double  $R \uparrow$   
 $h, w$  double  $R \downarrow$

$$C \propto \frac{\epsilon \cdot l}{d}$$

$L, \epsilon$  double  $C \uparrow$   
 $d$  double  $C \downarrow$


$$L \propto \ln\left(\frac{d}{w}\right) \cdot l$$

$d$  double  $L$  increases  
 $w$  double  $L$  decreases  
 $l$  double  $L$  doubles



$\epsilon$  = dielectric permittivity

4)	l doubles	w doubles	d doubles	h doubles	$\epsilon$ doubles	$\rho$ doubles
R	doubles	halves	—	halves	—	doubles
L	doubles	non-linear	—	non-linear	—	—
C	doubles	—	halves	doubles	doubles	—

 5: In HW2 Q4, we asked you to find the optimal number of inverters to drive a 100-unit load starting with a unit inverter. Repeat the problem minimizing delay using the Elmore delay model assuming now that due to interconnect, there is a  $2R$  (where  $R$  is the unit NMOS ON resistance) resistor between each inverter and its load as depicted below: (recall that a unit inverter has input capacitance  $C$  and thus a 100-unit load is equivalent to  $100C$  of capacitance)





5.) 1 stage.

  


$$D = (C \times R) + (100C \times 3R) = RC + 300RC = 301RC = 301\tau$$

2 stages

  

$$D = (C \times R) + (10C \times 3R) + (10C \times \frac{R}{10}) + (100C \times \frac{21}{10}R) = RC + 30RC + RC + 210RC = 242RC = 242\tau$$

3 stages

 

$$\text{Delay} = RC \left[ (1 \times 1) + (3 \times 4.64) + \left( 4.64 \times \frac{1}{4.64} \right) + (21.54 \times 2.216) + \left( 21.54 \times \frac{1}{21.54} \right) + (100 \times 2.046) \right]$$

$$= 269.25 RC = 269.25 \tau$$

Minimum<sup>delay</sup> = 2 stages.